


TI BYTE Simulation Exercise

Week 6 : Op-Amps


• Question 1:

1. Op amp is ideal. Gain from V_{IN} to V_{OUT} is:

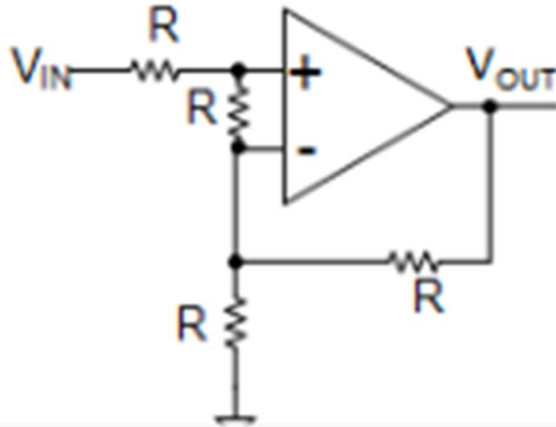- (a) 2
- (b) 4
- (c) 1
- (d) 1.5
- (e) 3
- (f) 2.5
- (g) 0
- (h) ∞



➤ QUCS Circuit:

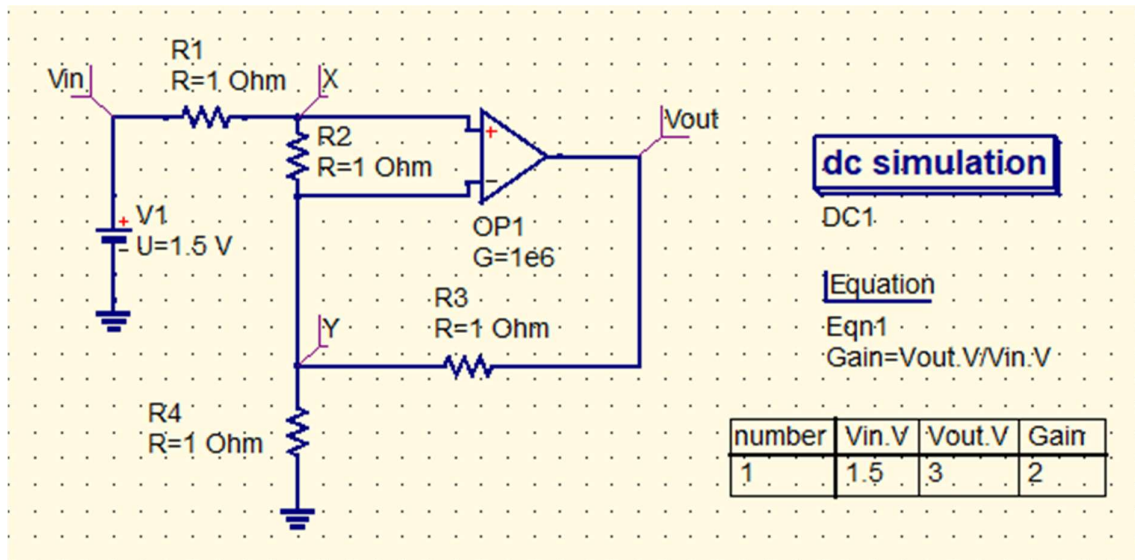

- V_{in} is the input voltage given with an amplitude of 1.5 V.
- V_{out} is used to label the output node and find the voltage at that node.
- The Op-Amp is considered to be an ideal one, but since an ideal Op-amp is difficult to implement in QUCS, the gain is considered to be very high ($\sim 10^6$), so that it behaves almost like an ideal one.

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

Thus, Gain = 2

Answer: (a)


➤ **Conclusion:**

- Since the Op-Amp is an ideal one and has infinite input impedance, no input current flows into the Op-Amp.
- Now, due to the presence of a negative feedback from the output of the Op-Amp to the inverting terminal of the Op-Amp, the voltage at the inverting and non-inverting terminal should be equal due to virtual short, i.e., $V_x = V_y$.
- Thus, there wouldn't be any current flowing through the resistor R2, and thus it can be ignored. So, the circuit simplifies into just a non-inverting amplifier.
- Now, since no current flows into the Op-Amp, no current flows through R1. Thus, $V_y = V_x = V_{in} = 1.5 \text{ V}$.
- So, current through R4, $I = \frac{V_y}{R_4} = \frac{1.5}{1} = 1.5 \text{ A}$
- Therefore, voltage at $V_{out} = V_y + I \times R_3 = 1.5 + 1.5 \times 1 = 3 \text{ V}$
- $Gain = \frac{V_{out}}{V_{in}} = \frac{3}{1.5} = 2$
- Thus, our answer is verified with the simulated result.


• **Question 2:**

11. I_1 and I_2 are equal current sources of value 1 mA. Op amp can be considered ideal. What is the voltage at V_o if $R = 0.5 \text{ k}\Omega$

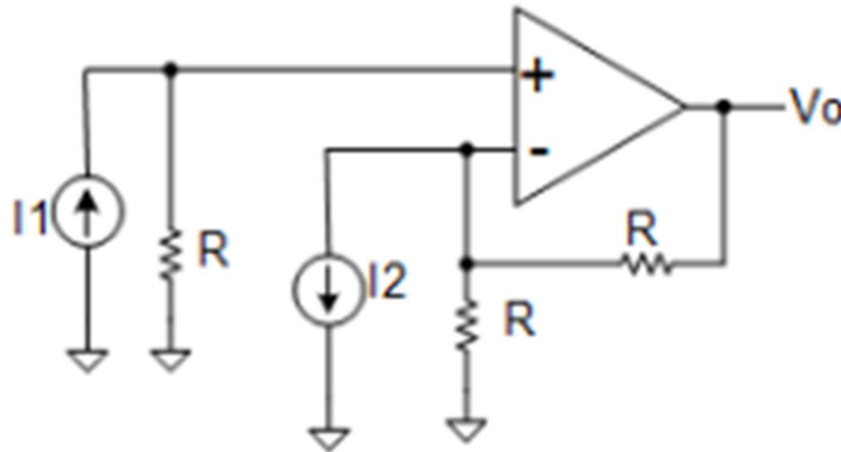- (a) 0.5V
- (b) -0.5V
- (c) 5V
- (d) 2V
- (e) 1V
- (f) 0V
- (g) 2.5V
- (h) 1.5V



➤ **QUCS Circuit:**

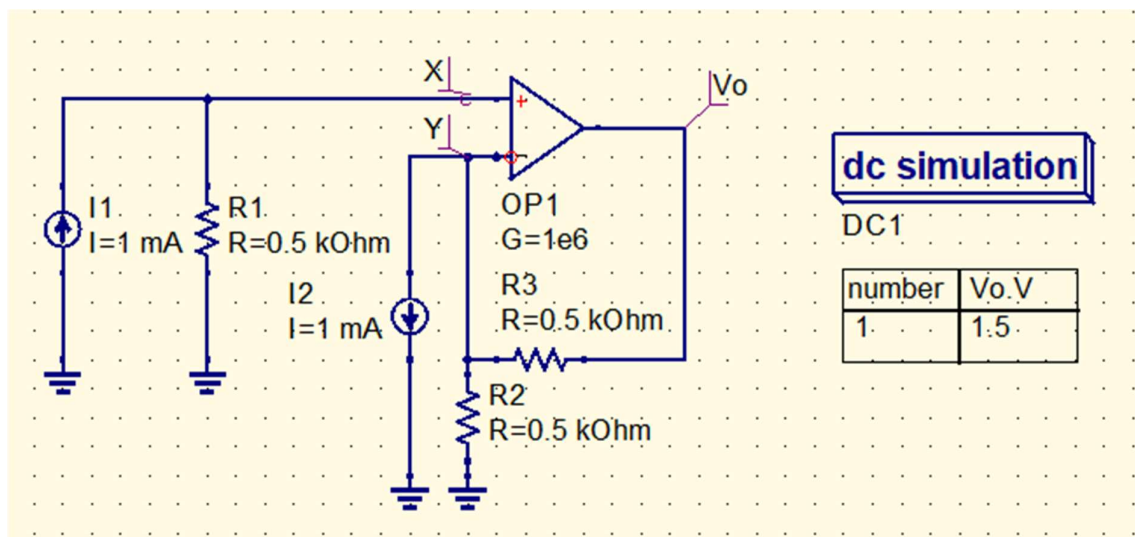

- The circuit has two current sources I_1 and I_2 , both of value 1 mA.
- V_{out} is used to label the output node and find the voltage at that node.
- The Op-Amp is considered to be an ideal one, but since an ideal Op-amp is difficult to implement in QUCS, the gain is considered to be very high ($\sim 10^6$), so that it behaves almost like an ideal one.

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

Thus, $V_o = 1.5 \text{ V}$

Answer: (h)

➤ **Conclusion:**

- Since the Op-Amp is an ideal one having infinite input impedance, no current can flow through it.
- Therefore, the current I_1 flows totally through R_1 , causing the voltage at node X to be, $V_x = I_1 R_1 = 0.5 \text{ V}$
- Due to the presence of a negative feedback from the output of the Op-Amp to the inverting terminal of the Op-Amp, the voltage at the inverting and non-inverting terminal should be equal due to virtual short, i.e., $V_x = V_y = 0.5 \text{ V}$
- Now, current through resistor R_2 , $I_3 = \frac{V_y}{R_2} = \frac{0.5}{0.5k} = 1 \text{ mA}$
- So, current flowing through R_3 , $I = I_2 + I_3 = 2 \text{ mA}$
- Then, $V_{out} = V_y + I \times R_3 = 0.5 \text{ V} + 2 \text{ mA} \times 0.5k\Omega = 1.5 \text{ V}$
- From the simulation, we got the same result, thus our answer is correct and verified.