


# TI BYTE Simulation Exercise

## Week 1 : RC Circuits


- Question 1:**

206. What is the final voltage on Node X?

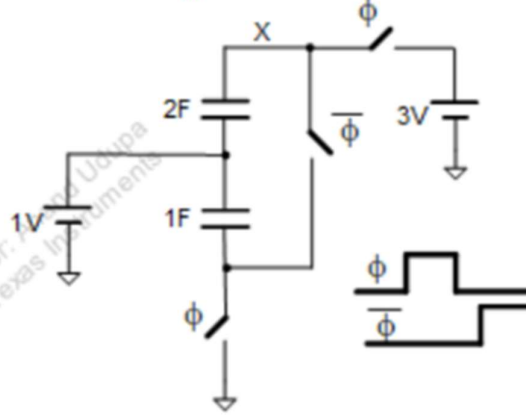- (a) -2V
- (b) -1V
- (c) 0V
- (d) 1V
- (e) 1.5V
- (f) 2V
- (g) 3V
- (h) 4V



➤ **QUCS Circuit:**

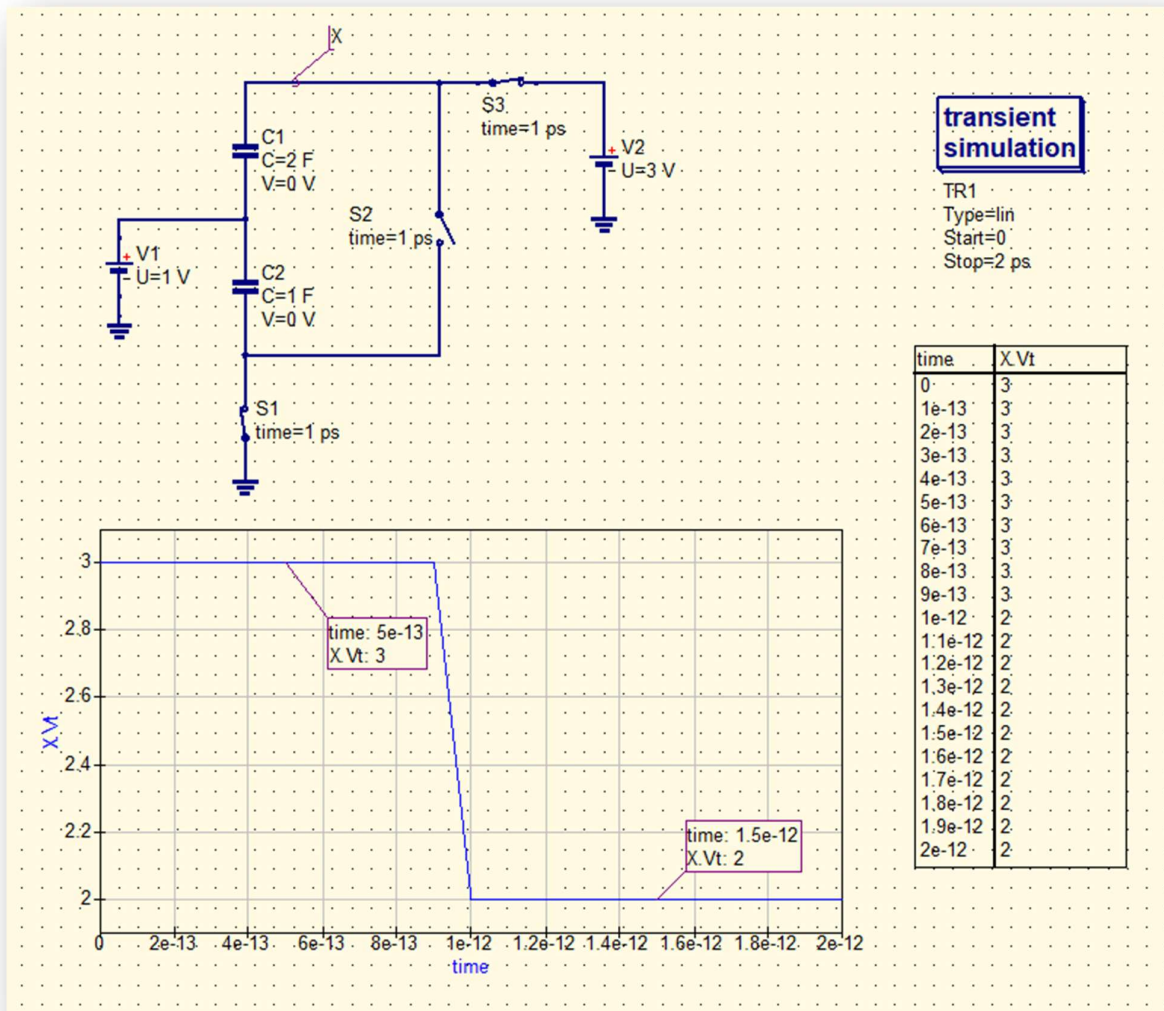

- **X is used to label the node and find the voltage at that node.**
- **Switches S1 and S3 are initially closed at  $t = 0$ , and S2 is opened.**
- **At  $t = 1$  ps, the switches S1 and S3 are opened, and switch S2 is turned closed.**

➤ **QUCS Result:**

**Therefore, from the simulation, we get our answer as:**

$$V_x = 2V$$

**Answer: (f)**


➤ **Conclusion:**

- **Since the resistance in these circuits are 0, the voltage sources provide Impulse currents, and thus the capacitors C1 and C2 are charged instantaneously at  $t = 0$ , up to 2V and 1V respectively.**
- **The voltage at X at  $t = 0$  is 3V.**
- **At  $t = 1$  ps, when S1 and S3 are opened and S2 is closed, the capacitors C1 and C2 share their charges and instantaneously arrive at a final voltage of  $V_x = 2V$ .**
- **The slope in the simulated Cartesian diagram at  $t = 1$  ps is due to the fact that, the step in the Transient simulation was taken as 0.1 ps.**


• **Question 2:**

204. The 2 switches in the circuit are initially closed and then opened. Voltage at node X after the 2 switches are opened is:

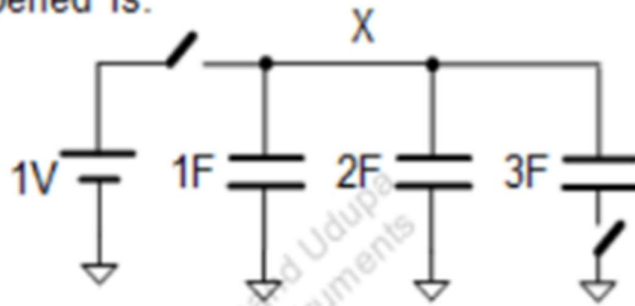- (a) 1V
- (b) 0V
- (c)  $\frac{1}{3}V$
- (d)  $\frac{1}{6}V$
- (e) 3V
- (f) 6V
- (g) 5V
- (h) 1.5V



➤ **QUCS Circuit:**

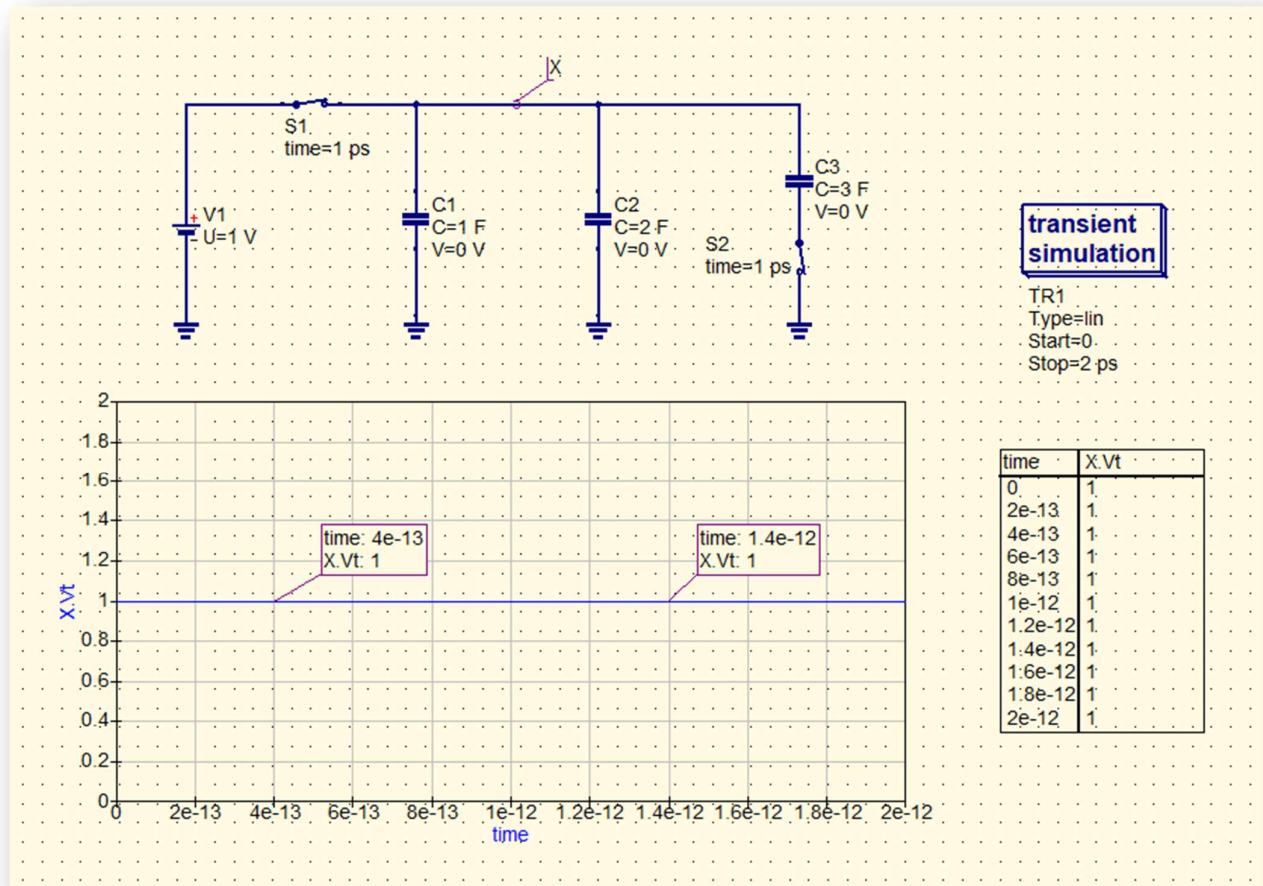

- The node X is used to find out the resulting voltage at that node.
- Switches S1 and S2 are initially closed at  $t = 0$ .
- At  $t = 1$  ps, the switches S1 and S2 are opened.

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

$$V_x = 1V$$

Answer: (a)

➤ **Conclusion:**

- Since the resistance in these circuits are 0, the voltage sources provide Impulse currents, and thus the capacitors C1, C2 and C3 all are charged instantaneously at  $t = 0$ , up to 1V.
- The voltage at X at  $t = 0$  is 1V.
- At  $t = 1$  ps, when S1 and S2 are opened, the lower plate of capacitor C3 becomes floating (or open-ended), and so no current flow will occur through that.
- Alongside, since both capacitors C1 and C2 both are charged up to 1V, thus no charge sharing occurs, its voltage remains at 1V. Thus the final voltage at node X is 1V.