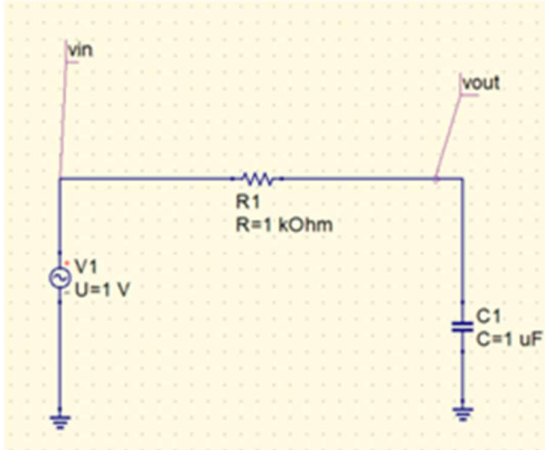


TI BYTE Simulation Exercise

Week 4 : RC Circuits with Voltage Sources

• Question 1:

- Make a first order RC circuit on QUCS as shown below:




We have analyzed this circuit in the simulator session.

Now replace the input sinusoidal with a pulse which has a peak value of 10 V and 50% duty cycle. Select a frequency such that the high and low periods in a pulse are both more than 10 times the time constant. What does this circuit function as?

- Repeat the experiment by now changing the frequency of the input pulse such that the high and low periods of the pulse are less than 10 times the time constant. What does this circuit function as?
Mathematically calculate what the response should look like and verify.


➤ QUCS Circuits and Results:

a) Sinusoidal input:

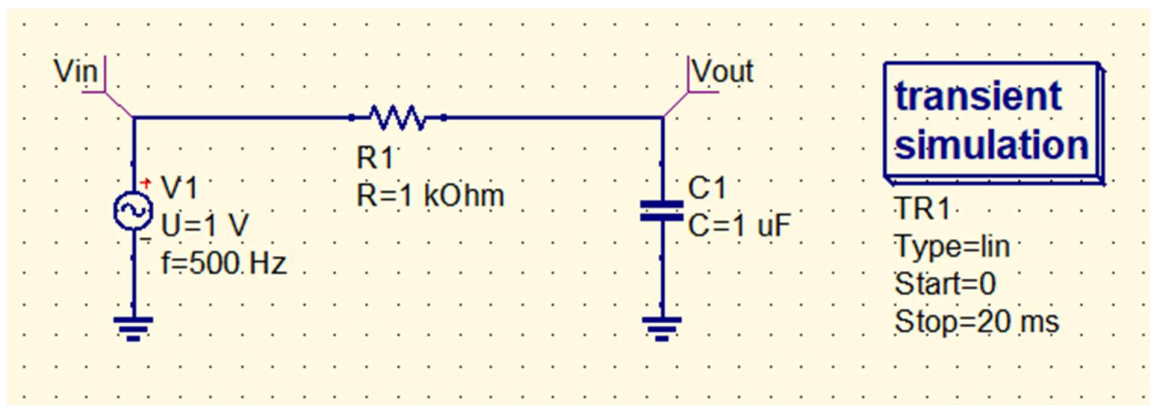


- The sinusoidal voltage source has an amplitude of 1 V and frequency of 1 Hz.

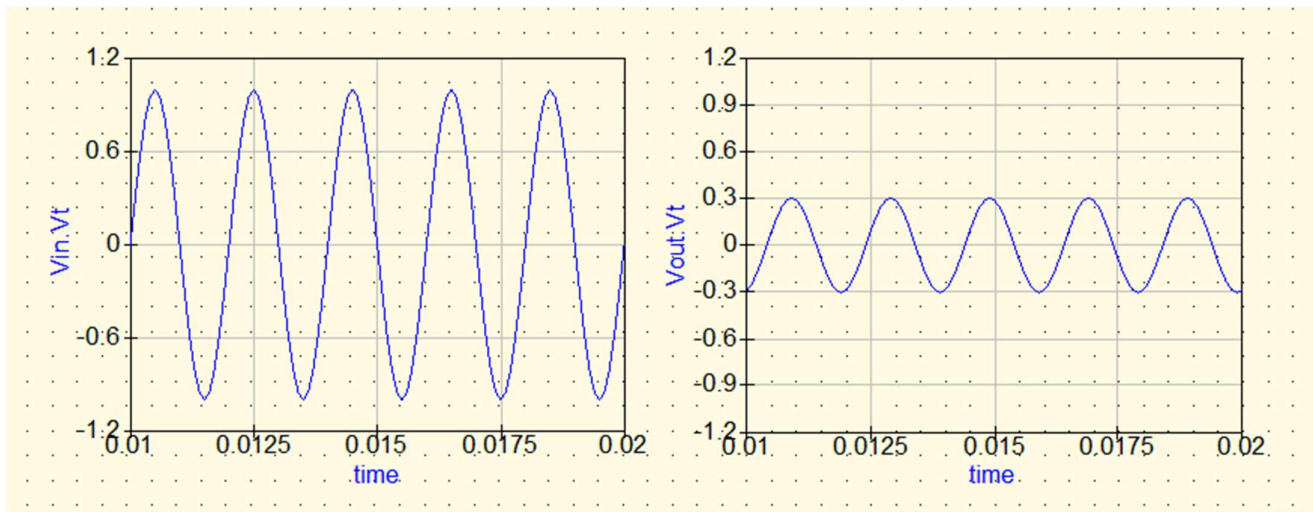The waveforms of the circuit look like the following:




b) Square input ($\tau > 10 RC$):

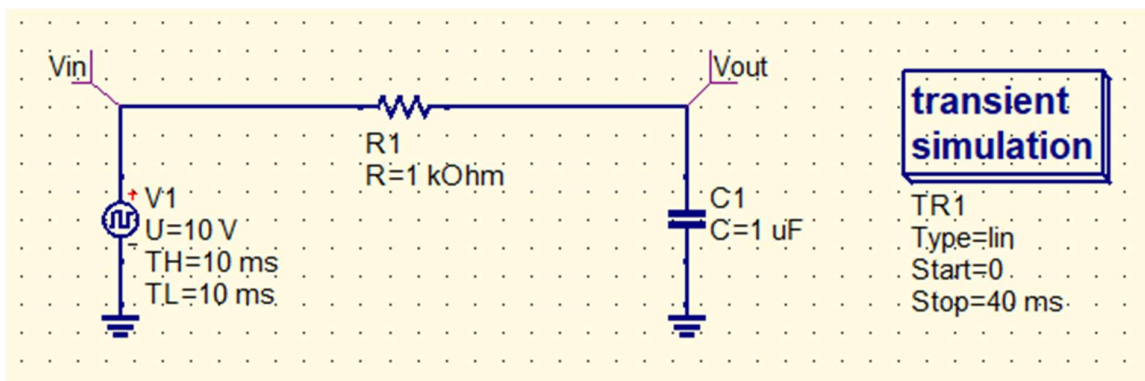

- The input sinusoidal voltage source is replaced with a pulse source with a frequency [evidently a square input].
- The square voltage source has an amplitude of 10 V and frequency of 50 Hz and 50% duty cycle. [Time period: 20 ms]
- The frequency is chosen such that the time period is more than 10 times the time constant of the circuit (1 ms).
- Thus, the capacitor has comparatively enough time to charge and discharge totally.
- The RC circuit, in the given circumstances, function as a Buffer, but with smooth rising and falling edges.
- The smoothness of the curve will depend on the ratio t/τ , higher the ratio, less smooth is the curve and vice versa.

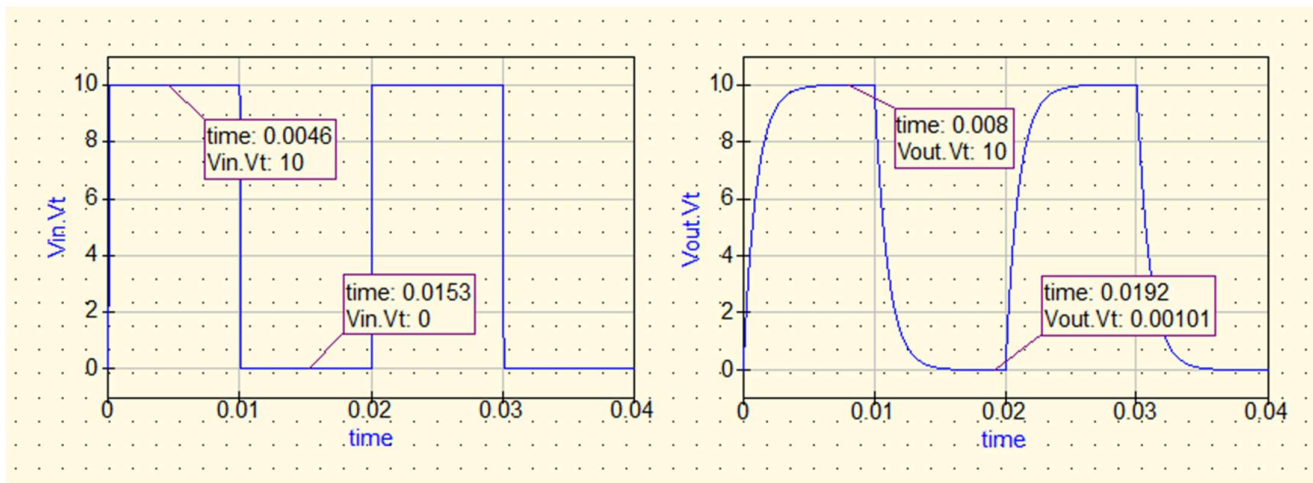The waveforms of the circuit look like the following:



➤ Calculations:

We have, $V_{in} = +10 \text{ V}$,

We know that the charging-discharging eqn. of the capacitor is:

$$V_c(t) = V_f + (V_i - V_f)e^{-t/\tau}$$

where V_f is the final voltage, V_i is the initial voltage and τ is the time constant $= RC = 1 \text{ ms}$.

For my circuit, the T_H of the pulse is comparatively high ($= 10 \text{ ms}$) and thus the capacitor will fully attain the steady state value which is 10 V , during this time. The calculations can be shown as follows:

$V_f = 10 \text{ V}$, $V_i = 0 \text{ V}$ and $\tau = 1 \text{ ms}$.

So, output capacitor voltage after 10 ms ,

$$\begin{aligned} V_c(t) &= [10 + (0 - 10)e^{-\frac{1}{1}}] \\ &= 10(1 - e^{-10}) \approx 10 \text{ V} \end{aligned}$$

Similarly for the T_L for the pulse, the capacitor will discharge completely through the resistor, as:


$V_f = 0 \text{ V}$, $V_i = 10 \text{ V}$ and $\tau = 1 \text{ ms}$.

So, output capacitor voltage after 10 ms ,

$$\begin{aligned} V_c(t) &= [0 + (10 - 0)e^{-\frac{10}{1}}] \\ &= 10e^{-10} \approx 0 \text{ V} \end{aligned}$$

Thus we can verify that the simulated output goes in accordance to the mathematically derived equation, and that, this circuit acts as a smooth buffer.

c) Square Input ($\tau < 10 RC$):

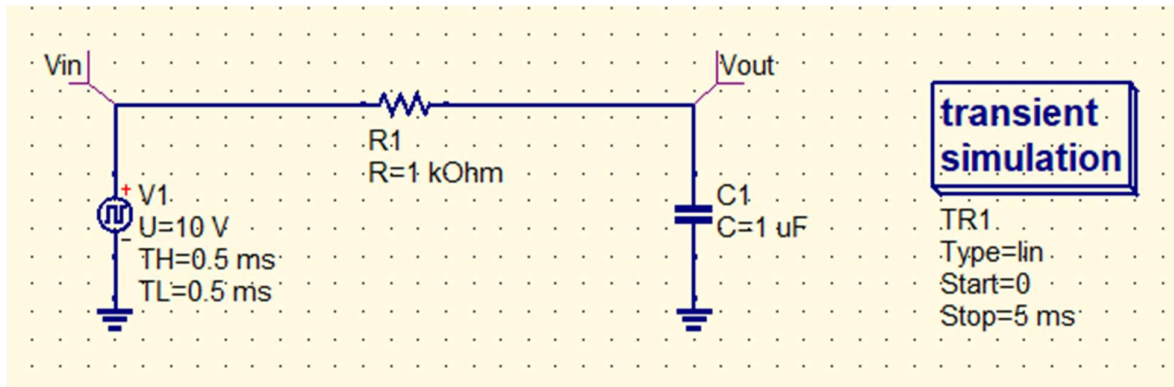

- The input sinusoidal voltage source is replaced with a pulse source with a frequency [evidently a square input].
- The square voltage source has an amplitude of 10 V and frequency of 1000 Hz and 50% duty cycle. [Time period: 1 ms]
- The frequency is chosen such that the time period is less than 10 times the time constant of the circuit (1 ms). [here, $t = \tau$]
- Since the time constant is much higher as compared to the time period, the rise and fall time for the charging and discharging curves will be high.
- Thus, the exponential curves of charging and discharging can thus be approximated as linear increasing and decreasing curves, with a V_{avg} value of $V_{peak}/2$.
- The RC circuit, in the given circumstances, function as an Integrator, where the square waveform is transformed into a triangular waveform.

➤ **Explanation:**

Since the capacitor charges very slowly, so for small values of t , all of the input voltage V_i will appear across the resistor. So, the current in the circuit will be

$$I(t) = \frac{V_i(t)}{R}$$

So, the output voltage across the capacitor,

$$V_o(t) = \frac{1}{C} \int I(t) dt = \frac{1}{C} \int \frac{V_i(t)}{R} dt = \frac{1}{RC} \int V_i(t) dt$$

The output is integrated version of the input voltage multiplied by a constant value.

➤ **Calculations:**

We have, $V_{in} = +10 \text{ V}$,

We know that the charging-discharging eqn. of the capacitor is:

$$V_c(t) = V_f + (V_i - V_f)e^{-t/\tau}$$

where V_f is the final voltage, V_i is the initial voltage and τ is the time constant = $RC = 1 \text{ ms}$.

- Now, for the first T_H time of the first cycle,

the voltage across the capacitor can be calculated as,

$V_f = 10 \text{ V}$, $V_i = 0 \text{ V}$ and $\tau = 1 \text{ ms}$, $T_H = 0.5 \text{ ms}$,

$$\begin{aligned} V_{out}(t) &= [10 + (0 - 10)e^{\frac{-0.5}{1}}] \\ &= 10(1 - e^{-0.5}) \approx 3.93 \text{ V} \end{aligned}$$

- After the first T_L time, V_{out} can be calculated as,

$V_f = 0 \text{ V}$, $V_i = 3.93 \text{ V}$ and $\tau = 1 \text{ ms}$, $T_L = 0.5 \text{ ms}$,

$$V_{out}(t) = [0 + (3.93 - 0)e^{\frac{-0.5}{1}}]$$

$$= 3.93e^{-0.5} \approx 2.38 \text{ V}$$

- In the next T_H of the next cycle,

$$V_f = 10 \text{ V}, V_i = 2.38 \text{ V and } \tau = 1\text{ms}, T_H = 0.5 \text{ ms},$$

$$V_{\text{out}}(t) = [10 + (2.38 - 10)e^{\frac{-0.5}{1}}]$$

$$= 10 - 7.62e^{-0.5} \approx 5.37 \text{ V}$$

- In the next T_L ,

$$V_f = 0 \text{ V}, V_i = 5.37 \text{ V and } \tau = 1\text{ms}, T_L = 0.5 \text{ ms},$$

$$V_{\text{out}}(t) = [0 + (5.37 - 0)e^{\frac{-0.5}{1}}]$$

$$= 5.37e^{-0.5} \approx 3.26 \text{ V}$$

- During the next T_H ,

$$V_f = 10 \text{ V}, V_i = 3.26 \text{ V and } \tau = 1\text{ms}, T_H = 0.5 \text{ ms},$$

$$V_{\text{out}}(t) = [10 + (3.26 - 10)e^{\frac{-0.5}{1}}]$$

$$= 10 - 6.74e^{-0.5} \approx 5.91 \text{ V}$$

- It can also be shown that at the final steady state response of the circuit can be equated, given that $T_H = T_L$,

The highest and the lowest peak value of the waveform are:

$$V_H = \frac{V}{2} \left(1 + \tanh \left(\frac{T_H + T_L}{4RC} \right) \right)$$

$$V_L = \frac{V}{2} \left(1 - \tanh \left(\frac{T_H + T_L}{4RC} \right) \right)$$


$$\text{For our case, } T_H = T_L = 0.5 \text{ ms}, RC = 1 \text{ ms},$$

$$\therefore, V_H = 5 \times (1 + \tanh(0.25)) = 5 \times (1 + 0.2249) = 6.224 \text{ V}$$

and, $V_L = 5 \times (1 - \tanh(0.25)) = 5 \times (1 - 0.2249) = 3.775 \text{ V}$

and, the average value of the triangular waveform is $= V_{in}/2 = 5 \text{ V}$

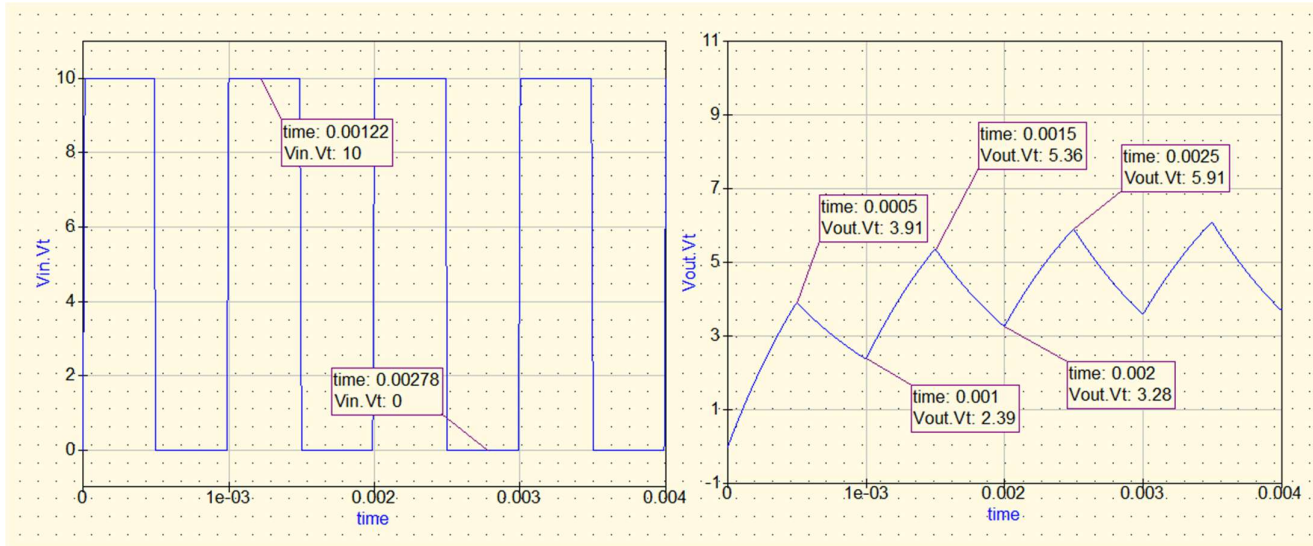The waveforms of the circuit look like the following:




➤ Conclusion:

The simulation result almost matches with our calculations. The slight difference in the values is because the input pulse is not an ideal one and there is some very small finite rise and fall times. Hence the T_H and T_L are not perfectly 1 ms. The output is approximately a triangular wave.

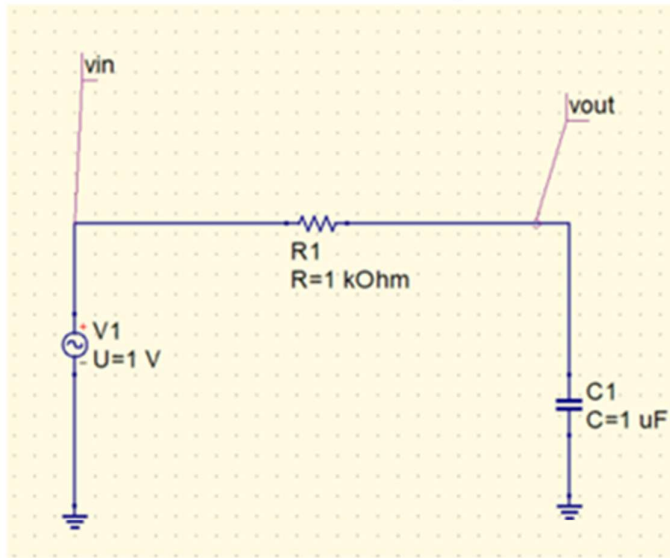• Question 2:

- Make a first order RC circuit on QUCS as shown below:



Replace the input sinusoidal with a ramp input [$x(t) = t \cdot u(t)$].

What do you think will happen?

What is the expected output at vout node? What does the simulator show?

➤ QUCS Circuits:

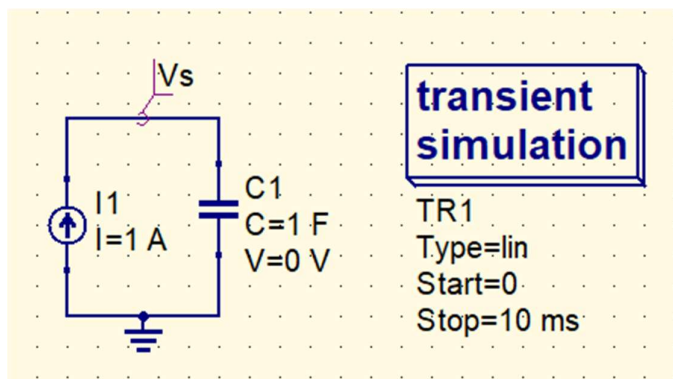


Fig 1. V ramp.sch

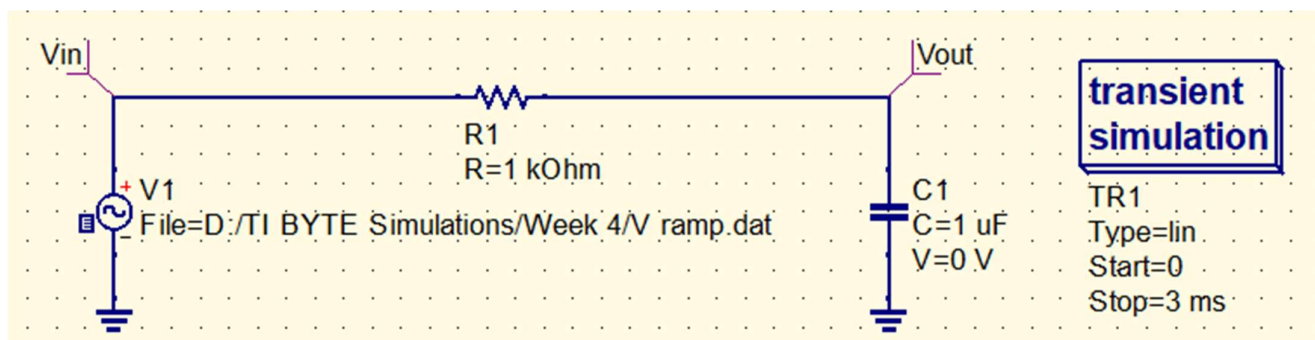


Fig 2. QUCS circuit using file-based voltage source

- The input sinusoidal voltage source is replaced with a ramp input source $[x(t) = t \times u(t)]$.
- Since ramp input source is not available, it is implemented using a file-based voltage source with the ramp voltage source implemented using a constant current source and a capacitor connected in series.
- The slope of the ramp voltage source $(\alpha) = 1$

➤ **Expected Output:**

- Initially, the capacitor will resist a change in its voltage as finite current flows through the circuit.
- So, all the voltage will appear across the resistor and the current in the circuit will be due to the voltage drop across the resistor which is the whole input voltage.
- So, the output voltage across the capacitor,

$$V_{out}(t) = \frac{1}{C} \int I(t) dt = \frac{1}{C} \int \frac{V_i(t)}{R} dt = \frac{1}{RC} \int V_i(t) dt$$

Here, $V_i(t) = \alpha t$, for $t > 0$

$$\text{So, } V_{out}(t) = \frac{\alpha}{RC} \int_0^t t dt = \frac{\alpha t^2}{2RC}$$

- Now, slowly the capacitor will start charging and the output voltage curve will be a parabolic one. (Integration of ramp)
- At steady state, capacitor behaves as an open circuit, so all of the voltage appears at the output and so at steady state, the output is a ramp with the same slope.
- So, the resultant output is a delayed ramp. This delay is given by αRC , where α is the slope of the ramp (here, 1).
- In this case, the delay is equal to the time constant $= 1\text{ms}$.


$$V_{out} = \alpha t - \alpha RC \left(1 - e^{-t/RC}\right)$$

$$V_{out} = \alpha(t - RC) + \alpha RC e^{-t/RC}$$

$$\text{If } \tau \gg RC, \quad V_{out} \approx \alpha(t - RC)$$

➤ QUCS Result:

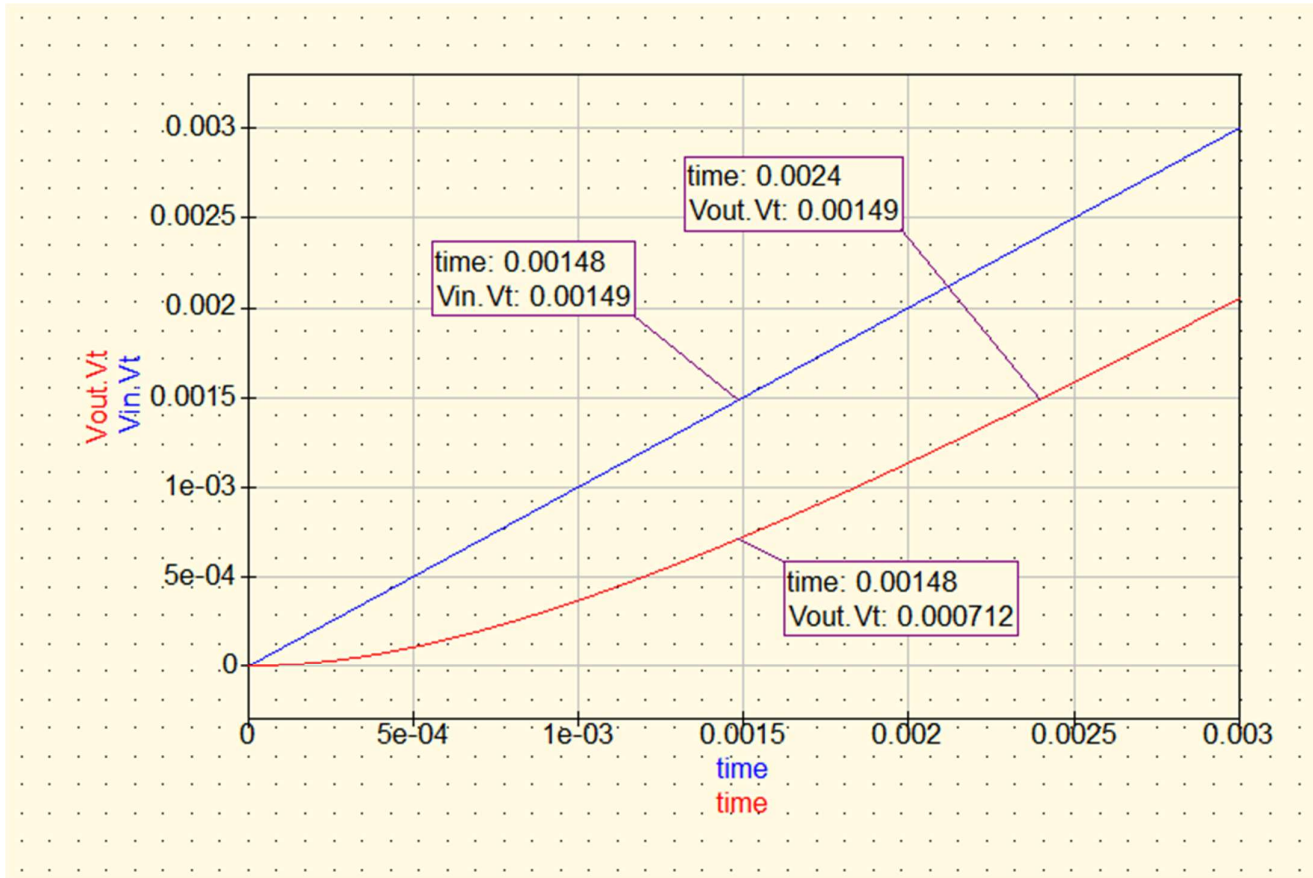The output waveform of the RC circuit with a Ramp input using QUCS looks like the following,



➤ Conclusion:

- From the simulation, we see that the output is initially following a parabolic curve and at steady state it attains a ramp state.
- Thus, the resultant output is a delayed ramp.
- V_{in} and V_{out} both attain 0.00149 V but the time delay is given by $(0.0024 \text{ s} - 0.00148 \text{ s}) = 0.00092 \text{ s}$ or 0.92ms, which verifies our calculation.