


TI BYTE Simulation Exercise

Week 0 : Voltage and Current Sources


- Question 1:**

103. V_X and I_X are respectively:

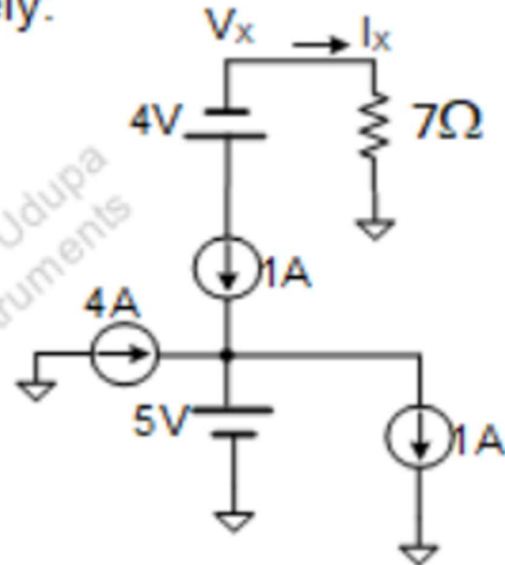- (a) 4V, 1A
- (b) -4V, -1A
- (c) 4V, -1A
- (d) -7V, -1A
- (e) 7V, 4A
- (f) 1V, 4A
- (g) -1V, -4A
- (h) Not a valid circuit



➤ **QUCS Circuit:**

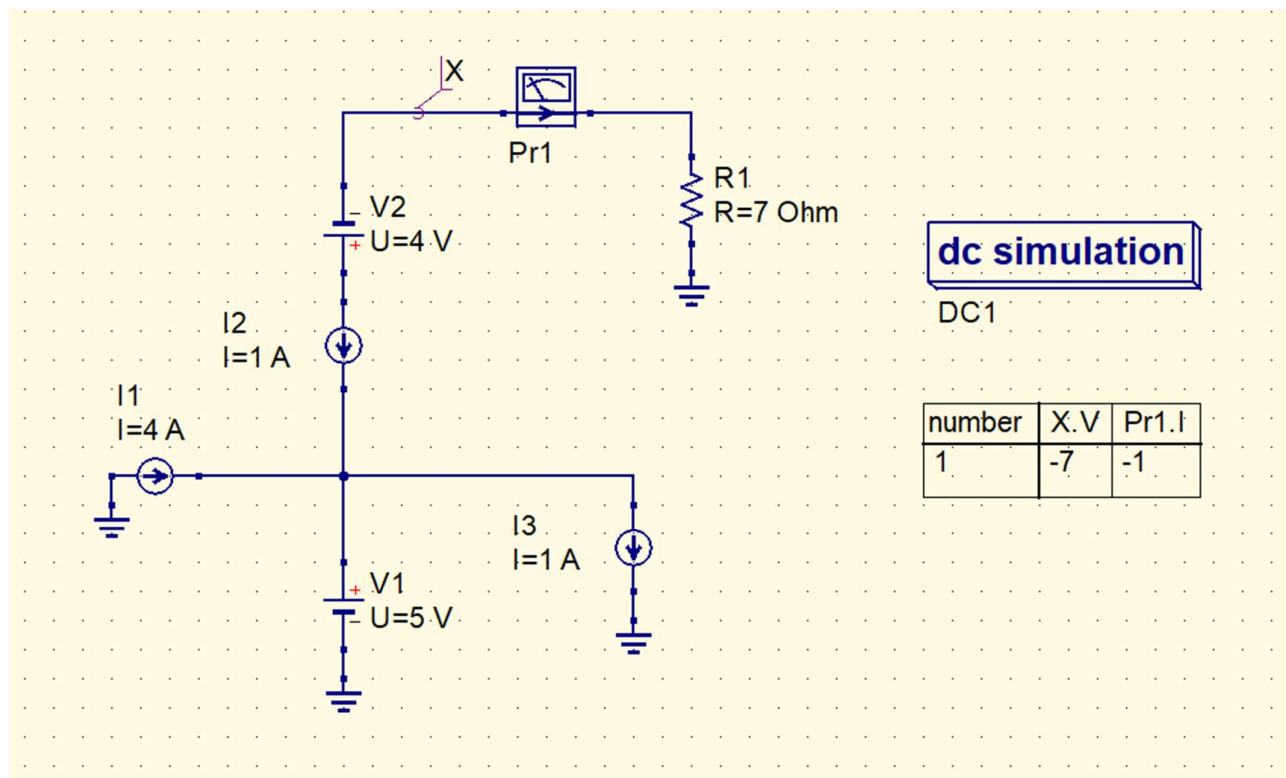

- **X is used to label the node and find the voltage at that node.**
- **Current probe (Pr1) is used to check the current through that wire.**

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

$$V_x = -7V$$

$$I(\text{Pr1}) = -1A$$

Answer: (d)


➤ **Conclusion:**

- **In a series circuit, the current that flowing through each component is the same.**
- **A voltage source and a current source in series is equivalent to a current source in series.**


• **Question 2:**

309. For the DAC circuit shown, what is V_{out} for the digital input $D3=1$, $D2=0$, $D1=1$, $D0=0$, if $V_{ref}=8V$, where V_{ref} is the reference voltage for the DAC.

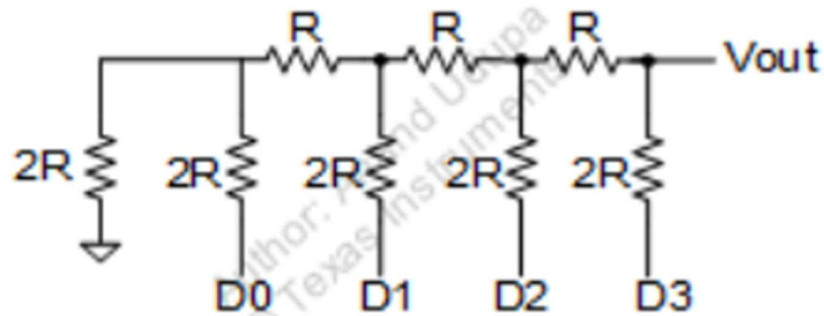- (a) 6V
- (b) 2V
- (c) 8V
- (d) 4V
- (e) 7V
- (f) 3V
- (g) 1V
- (h) 5V



➤ **QUCS Circuit:**

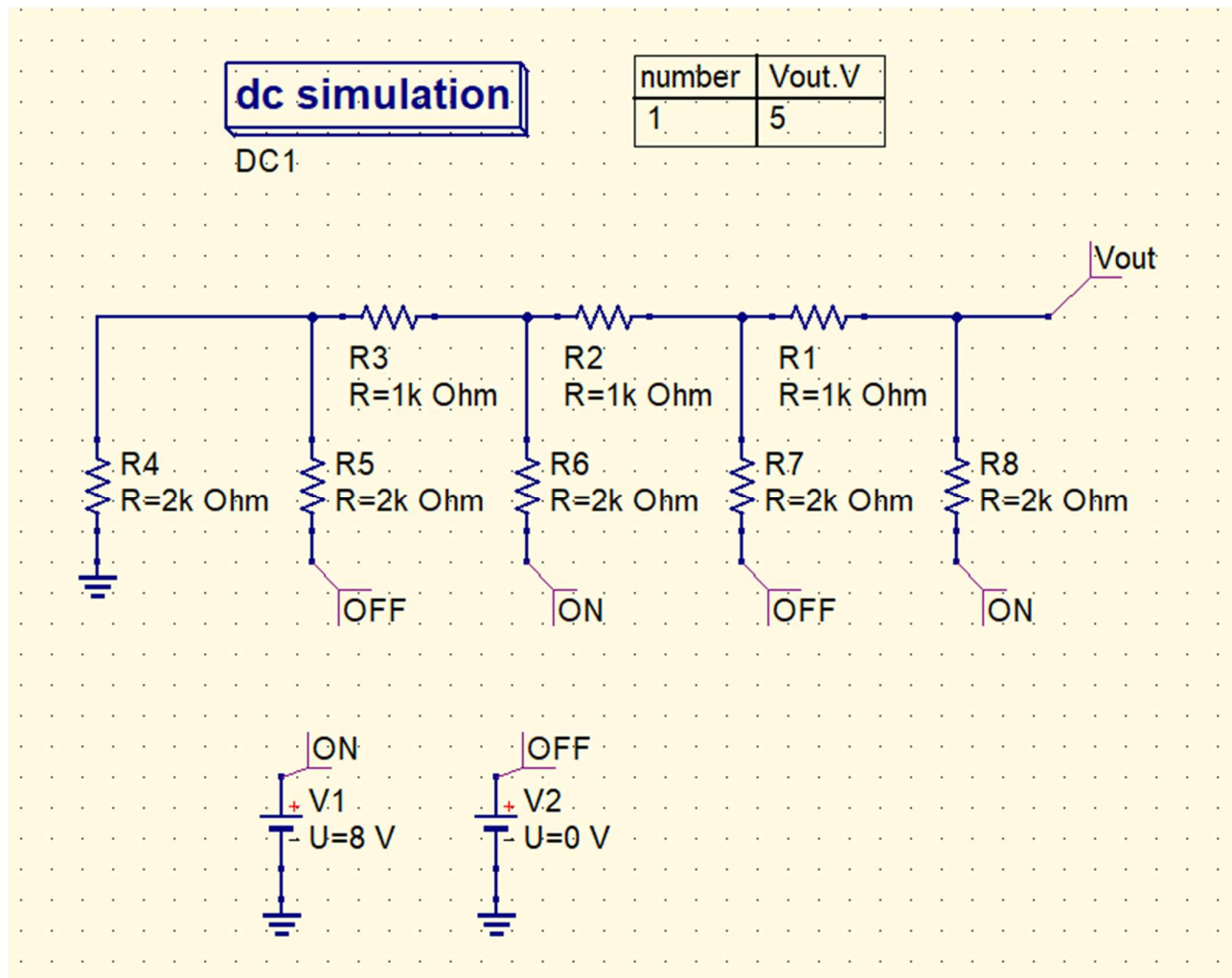

- The node V_{out} is used to find out the resulting voltage at that node.
- The nodes ON is used to signify a Digital value of 1 (Analog equivalent voltage of 8 V (V_{ref})).
- The nodes OFF is used to signify a Digital value of 0 (Analog equivalent voltage of 0 V (Ground)).

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

$$V_{out} = 5V$$

Answer: (h)

➤ **Conclusion:**

- A Resistance-ladder can be minimized into a simple circuit using the Thevenin theorem or the Norton theorem.
- The superposition theorem can also be applied to simplify the complex ladder.
- A voltage source (V) and a resistor (R) in series can be converted into its Norton equivalent, a current source (I) and a resistance (R') in parallel, by:

$$I = \frac{V}{R} ;$$

$$\text{and, } R' = R$$