


TI BYTE Simulation Exercise

Week 3 : RL Circuits


• Question 1:

603. $V_s = 2.u(t)$. $I_s = 4.u(t) - 3u(t-1)$. Voltage at node X at $t = 0.5\text{sec}$ is:

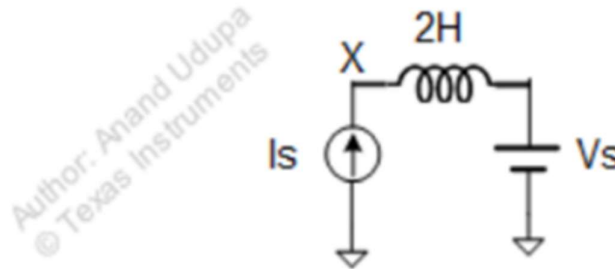- (a) 2V
- (b) ∞ V
- (c) 6V
- (d) 3V
- (e) 0V
- (f) 4V
- (g) 1V
- (h) 10V




➤ QUCS Circuit:

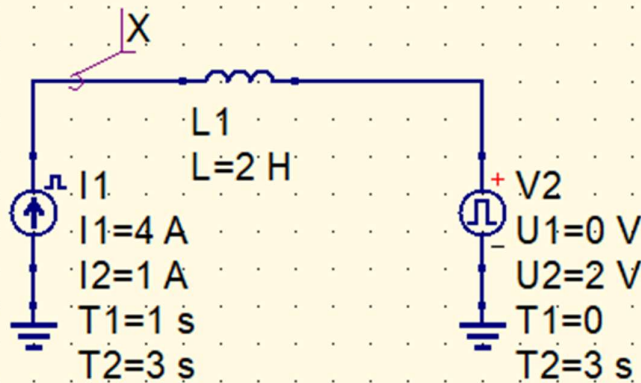

**transient
simulation**

TR1
Type=lin
Start=0
Stop=1 s

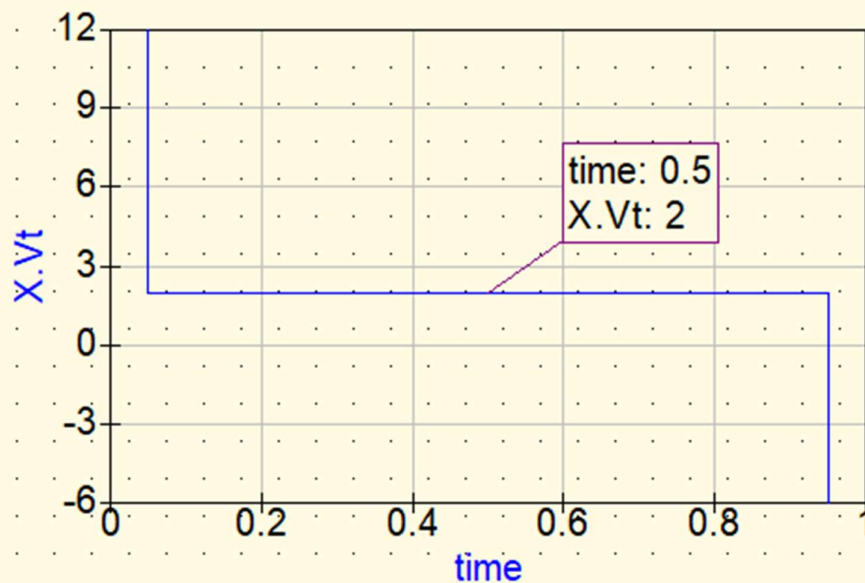

time	$X.Vt$
0.5	2

- **X is used to label the node and find the voltage at that node.**
- **Both the inductors have zero initial current through them.**

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

$$V_x = 2V$$

Answer: (a)

➤ **Conclusion:**

- **The final voltage at X can be found out using the Superposition Theorem.**
- **Upon considering the current source I1 only,**

$$I_1 = 4 \cdot u(t) - 3 \cdot u(t - 1)$$

$$I_1 = \begin{cases} 4, & 0 \leq t \leq 1 \\ 1, & t > 1 \end{cases}$$

- **Thus, voltage across the inductor due to the current source only,**

$$V_L = L \frac{dI}{dt}$$

$$I_1 = \begin{cases} \delta(t), & t = 0 \\ -\delta(t), & t = 1 \\ 0, & \text{elsewhere} \end{cases}$$


- **Due to the voltage source V2, the voltage at X is 2V.**
- **Therefore, it can be said that, at t = 0.5s, the voltage at X is**

$$V_x = V_L + V_2 = (0 + 2) V = 2V.$$


• **Question 2:**

610. $V(t) = u(t)$. What is the steady state value of the voltage across the 1 nH inductor?

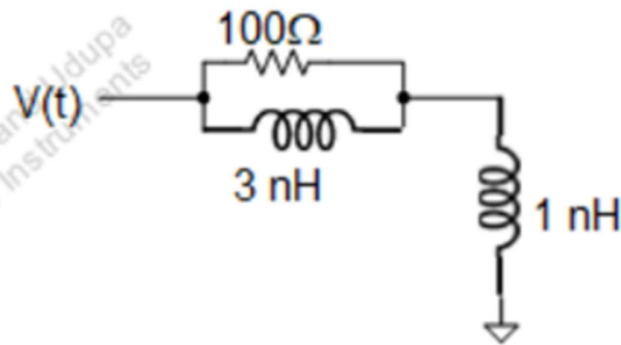- (a) 0V
- (b) 0.5V
- (c) 1V
- (d) 2V
- (e) 1.5V
- (f) 0.25V
- (g) 1.25V
- (h) 0.75V




➤ **QUCS Circuit:**

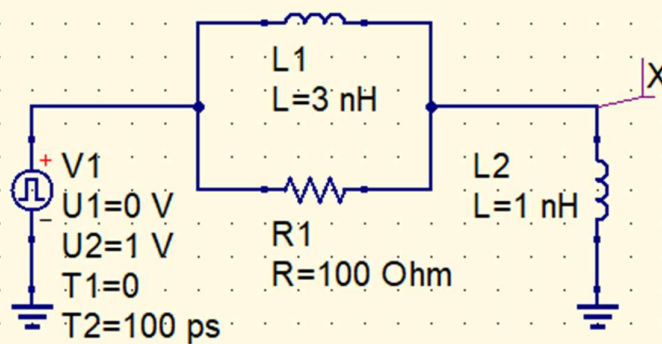

**transient
simulation**

TR1
Type=lin
Start=0
Stop=80 ps

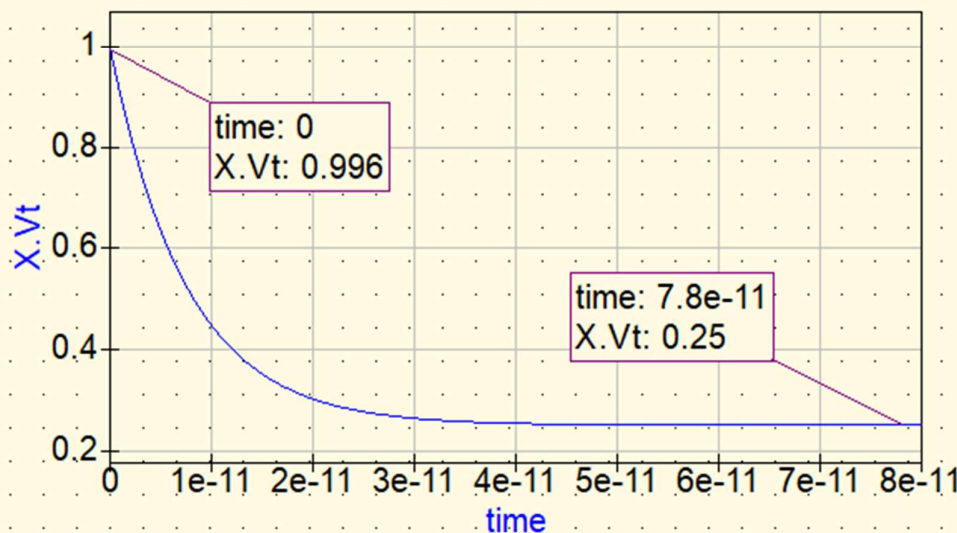

time	X.Vt
8e-11	0.25

- X is used to label the node at which the unknown voltage is to be determined.

- Both the inductors L1 and L2 are initially uncharged, i.e., having zero initial current in them.

➤ **QUCS Result:**

Therefore, from the simulation, we get our answer as:

$$V_x = 0.25V$$

Answer: (f)

➤ **Conclusion:**

- At $t = 0$, since both the inductors are uncharged, they have high impedances and behave as open circuits (o.c.).
- Thus, no current flows through them, or even through the R1.
- Therefore, the voltage at node X is

$$V_x \approx V_1 = 1V$$

- Now, at $t = \infty$, both the inductors have reached steady state and have low impedance and behave as almost short circuits (s.c.).
- Since the current gets low impedance path through L1, the equivalent impedance becomes,

$$L_1 || R_1 \approx L_1$$

- Thus, the voltage at X at $t = \infty$ (), is just a voltage divider between L1 and L2,

- The final voltage at X = $\frac{L_2}{L_1 + L_2} = \frac{1}{(1+3)} = \frac{1}{4} = 0.25 V$